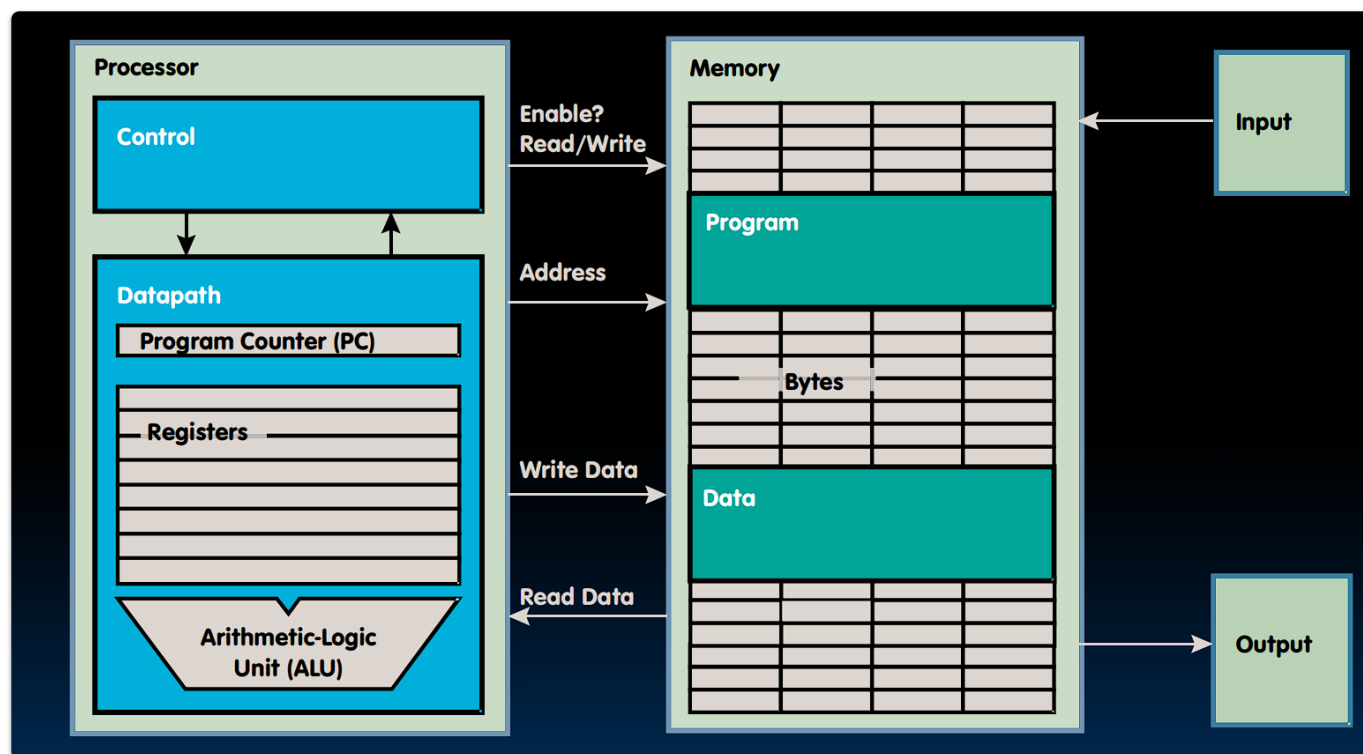


# Single-Core Processor



## CPU

The active part of the computer that does all the work.

- Data manipulation.
- Decision making.

## Datapath

Portion of the processor that contains hardware necessary to perform operations required by the processor (the body)

## Control

Portion of the processor that tells the datapath what needs to be done.(the brain)

# One-Instruction-Per-Cycle RISC-V Machine


## Stage of the Datapath

---

break up the process of "executing an instruction" into stages, and then connect the stages to create the whole datapath.

- **Stage 1: *Instruction Fetch (IF)***
- **Stage 2: *Instruction Decode (ID)***
- **Stage 3: *Execute (EX) - ALU (Arithmetic-Logic Unit)***
- **Stage 4: *Memory Access (MEM)***
- **Stage 5: *Write Back to Register (WB)***

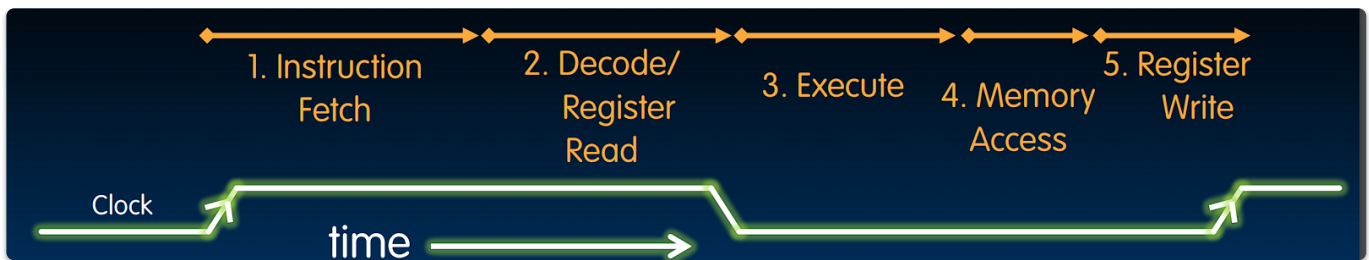These five stages are executed in one clock cycle, which is called One-instruction-Per-cycle.




Register write will be executed at the next rising edge of clock.

## Datapath components

### COMBINATIONAL

- Combinational elements

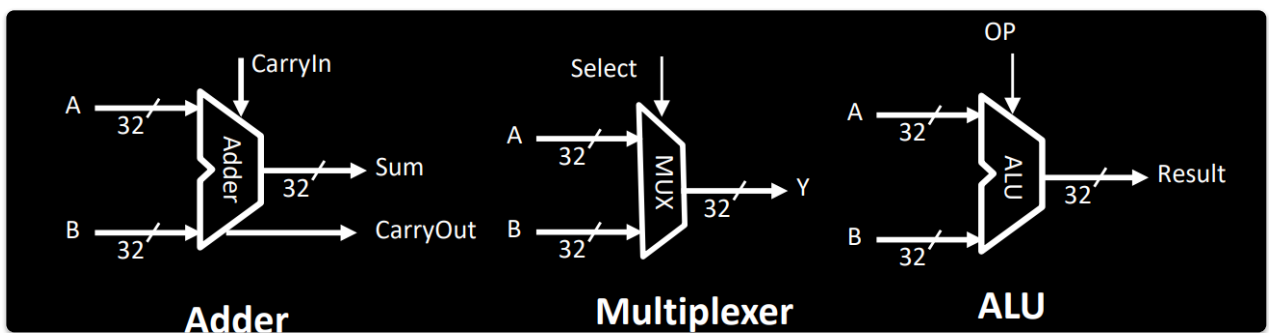


### STATE AND SEQUENCING

#### Register

- Register

- Write Enable:

 - Low (or deasserted) (0): Data Out will not change
- Asserted (1): Data Out will become Data In on positive edge of clock



## Register File

Consists of 32 registers

- Register file (regfile, RF) consists of 32 registers:


- Two 32-bit output busses: busA and busB
- One 32-bit input bus: busW

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (Clk)

 - Clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
  - RA or RB valid  $\Rightarrow$  busA or busB valid after “access time.”



## Memory

- “Magic” Memory


- One input bus: Data In
- One output bus: Data Out

- Memory word is found by:

- For Read: Address selects the word to put on Data Out
- For Write: Set Write Enable = 1: address selects the memory word to be written via the Data In bus

- Clock input (CLK)

 - CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block: Address valid  $\Rightarrow$  Data Out valid after “access time”



For **read** operation we **don't** need to wait for the clock, just put the address of register or memory, the data will automatically pop up.

For **write** operation we need to wait for the rising edge of the clock to write data.

Each instruction during execution reads and updates the state of

1. registers
2. pc
3. Memory

## Datapath

### R-Format Datapath

---

# Review

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
R-format : ALU																															
[31:25]							[24:20]					[19:15]					[14:12]			[11:7]					[6:0]						
7							5					5					3			5					7						
func7							rs2					rs1					func3			rd					opcode						
0000000							rs2					rs1					000 : ADD			rd					0110011:OP-R						
0100000							rs2					rs1					000 : SUB			rd					0110011:OP-R						
0000000							rs2					rs1					001 : SLL			rd					0110011:OP-R						
0000000							rs2					rs1					010 : SLT			rd					0110011:OP-R						
0000000							rs2					rs1					011 : SLTU			rd					0110011:OP-R						
0000000							rs2					rs1					100 : XOR			rd					0110011:OP-R						
0000000							rs2					rs1					101 : SRL			rd					0110011:OP-R						
0100000							rs2					rs1					101 : SRA			rd					0110011:OP-R						
0000000							rs2					rs1					110 : OR			rd					0110011:OP-R						
0000000							rs2					rs1					111 : AND			rd					0110011:OP-R						

- E.g. Addition/subtraction **add rd, rs1, rs2**  
 $R[rd] = R[rs1] + R[rs2]$   
**sub rd, rs1, rs2**  
 $R[rd] = R[rs1] - R[rs2]$

Garcia, Nikolai

Berkeley UNIVERSITY OF CALIFORNIA

RISC-V (20)

CC BY NC

## Implementing the add instruction

31	25	24	20	19	15	14	12	11	7	6	0																				
funct7							rs2					rs1					funct3			rd					opcode						
7							5					5					3			5					7						
0000000							rs2					rs1					000			rd					0110011						
7							5					5					3			5					7						
add							rs2					rs1					add			rd					Reg-Reg OP						



**add rd, rs1, rs2**

Instruction does two changes

- Reg[rd] = Reg[rs1] + Reg[rs2]**


## 2. PC +=4

### DATAPATH FOR ADD

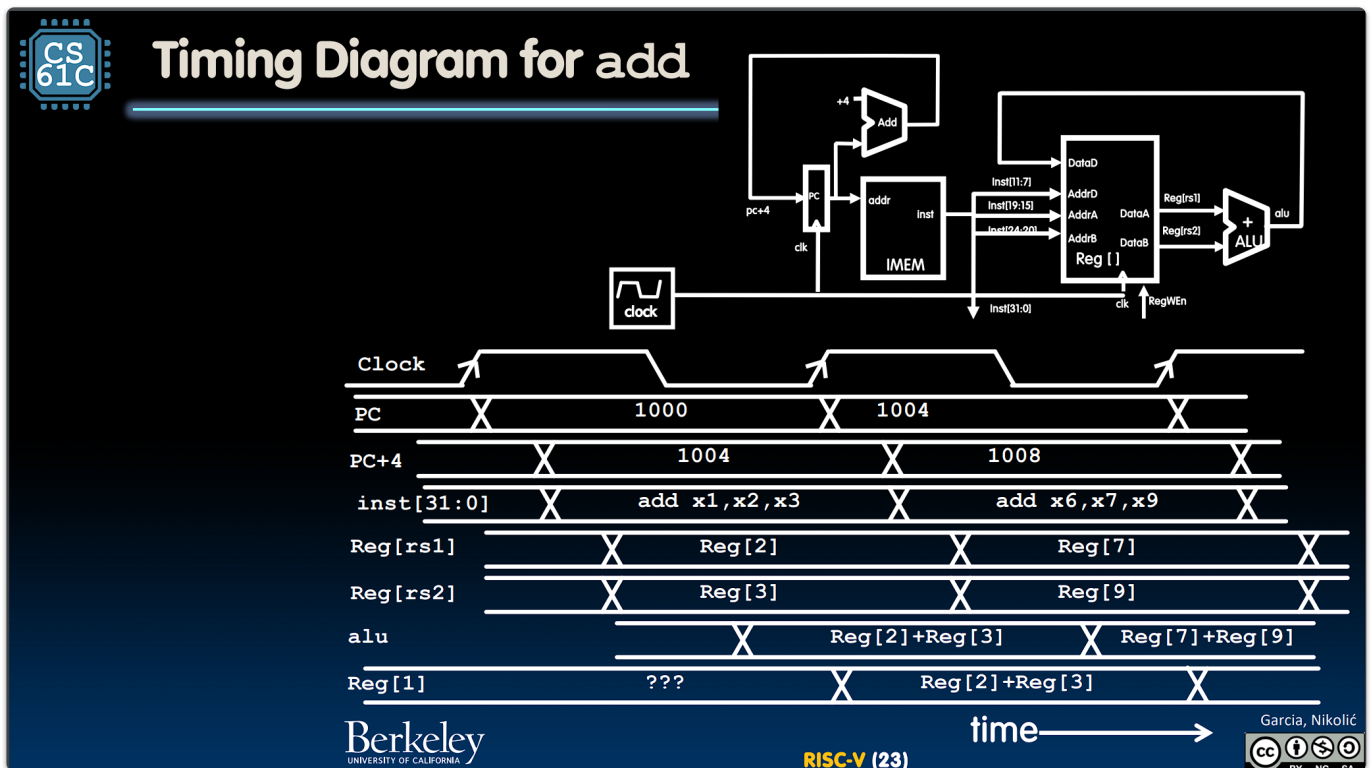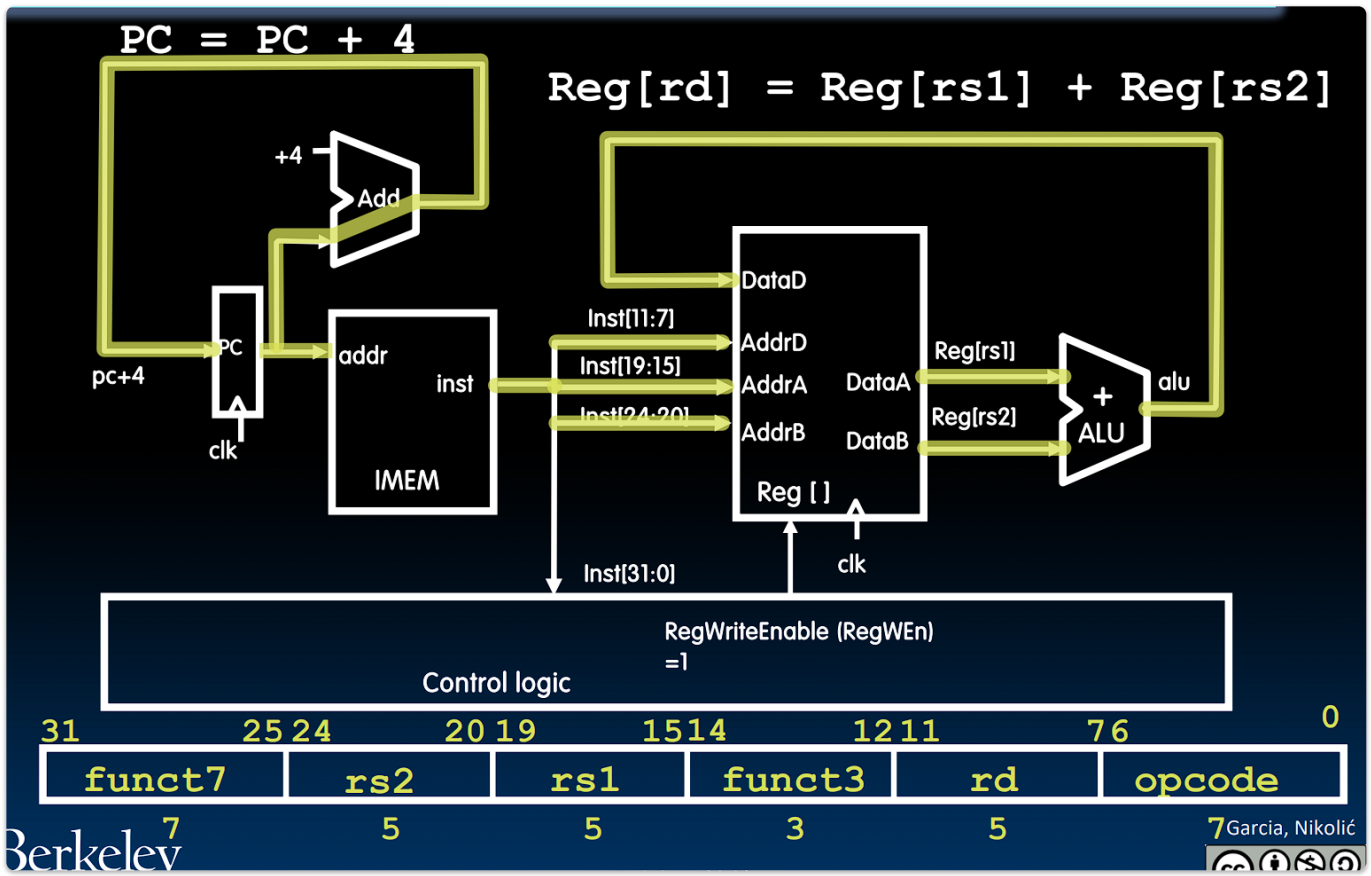
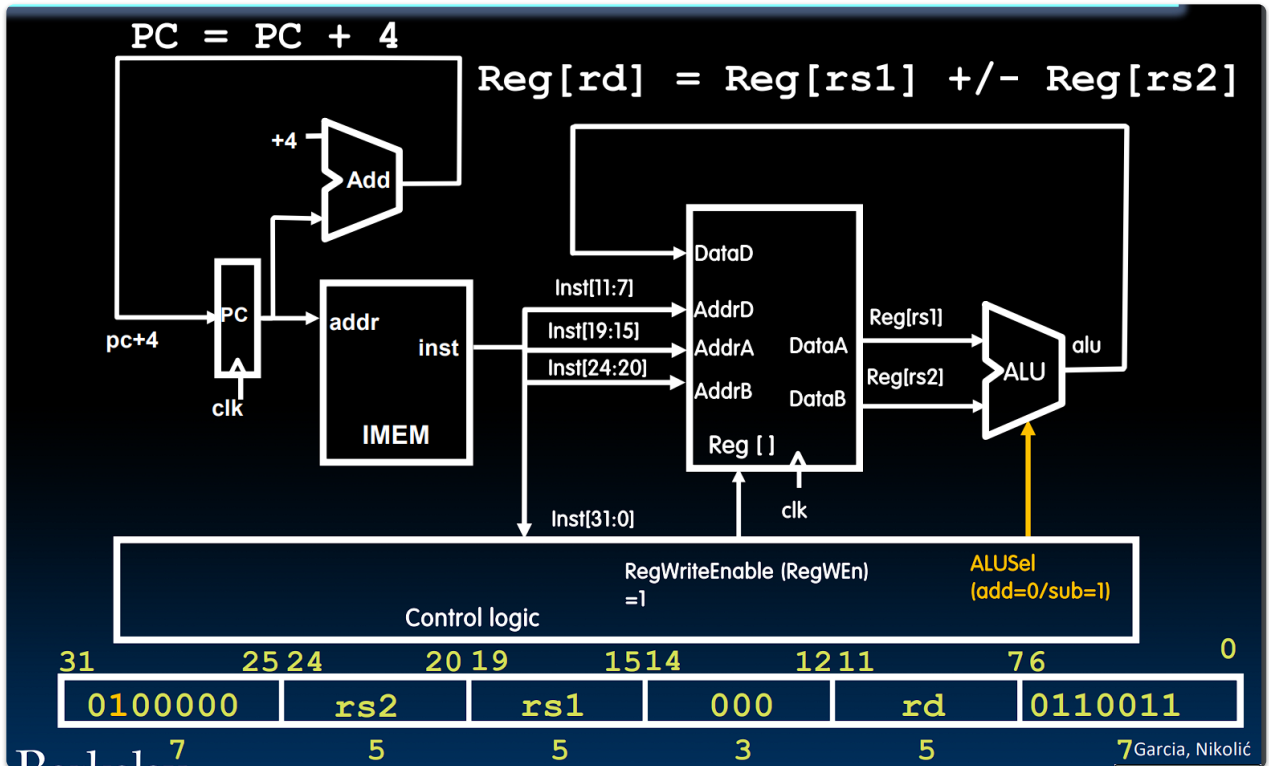
## DATAPATH FOR SUB/ADD

- sub almost the same as add, except now we need to subtract operands.




## I-Format Datapath

### Addi




# Datapath for add/sub


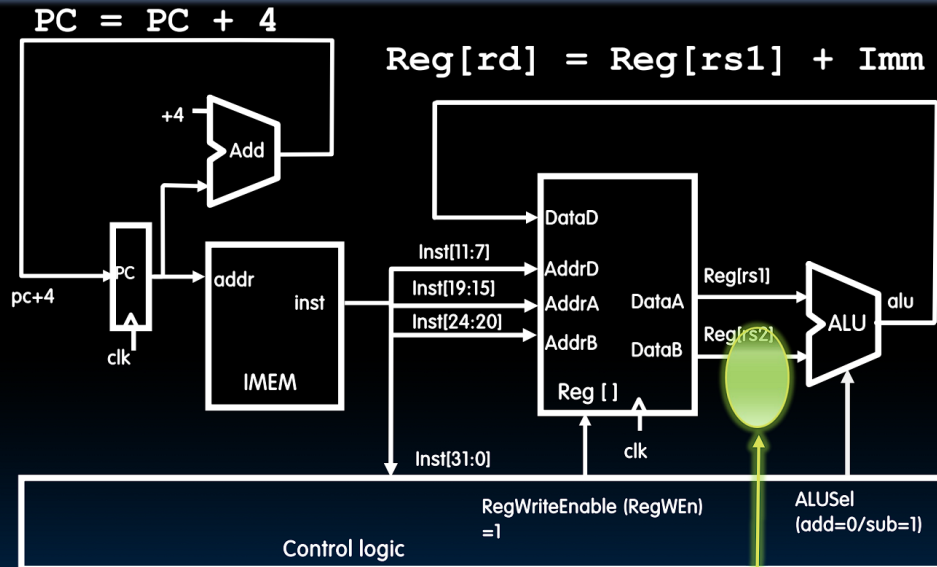



Immediate should be here

Add a Mux at there

# Adding addi to Datapath

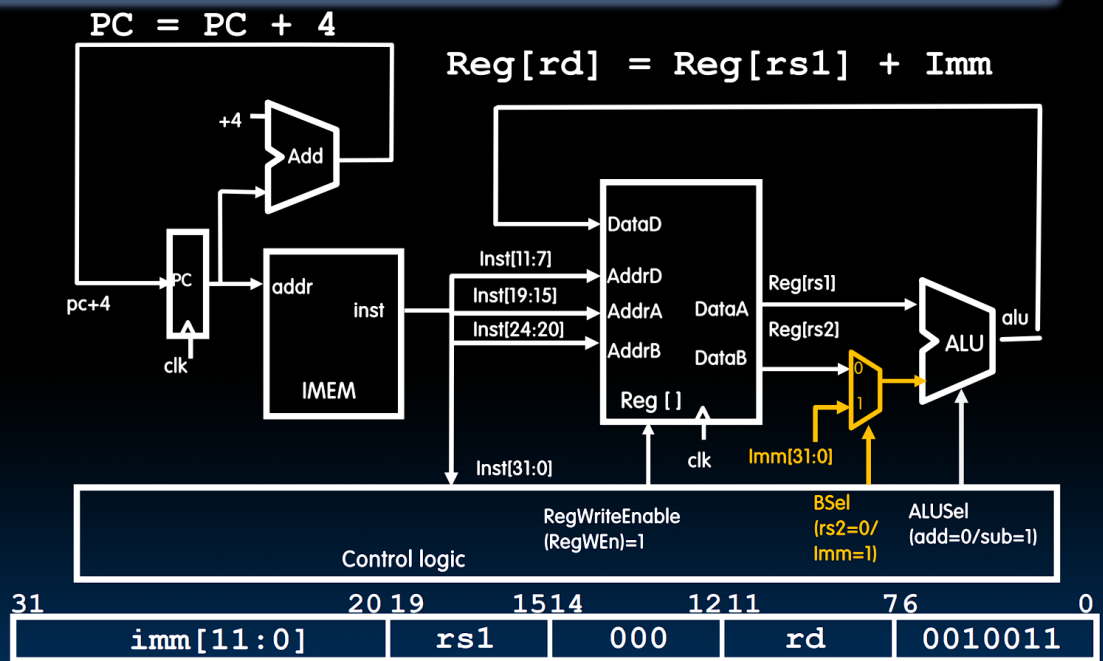


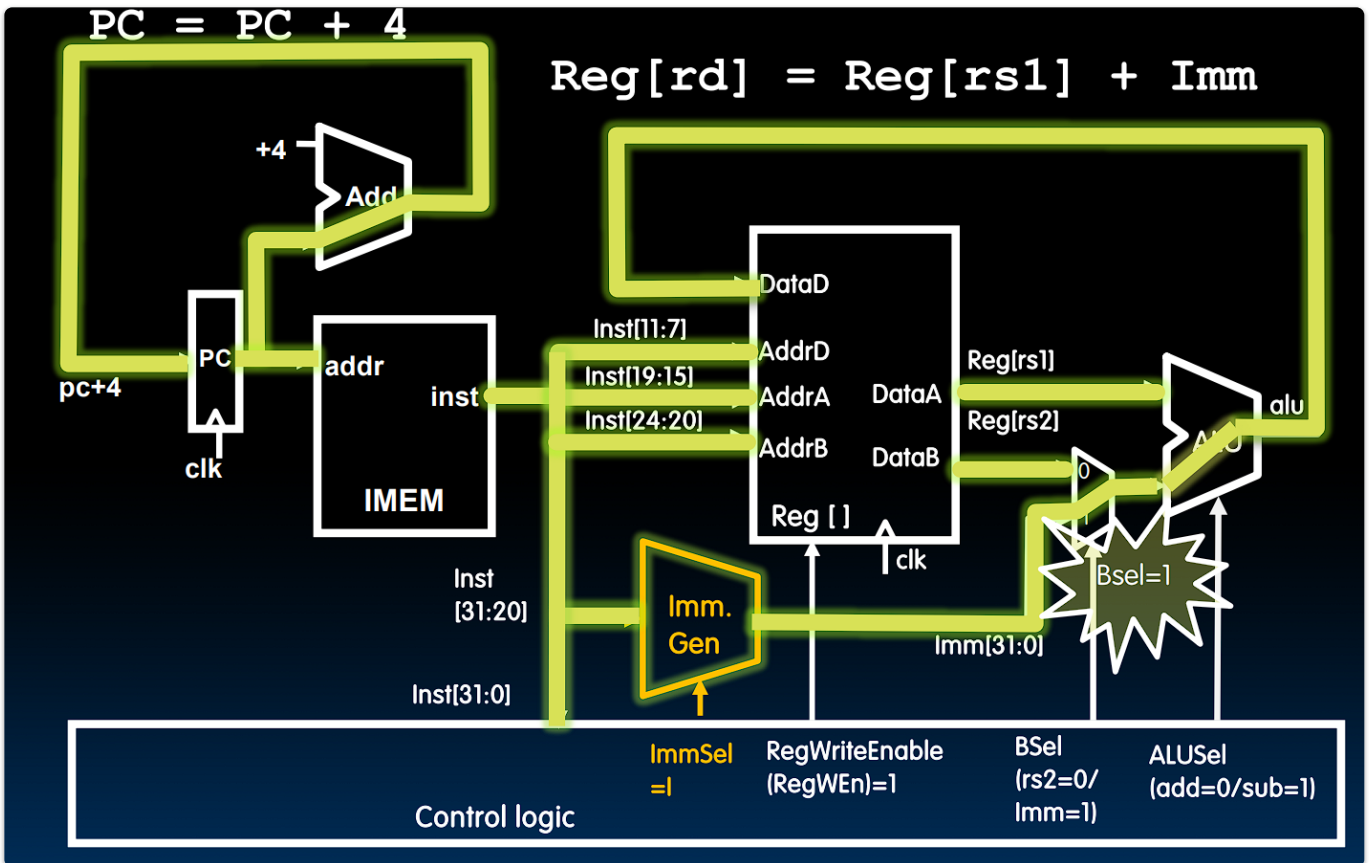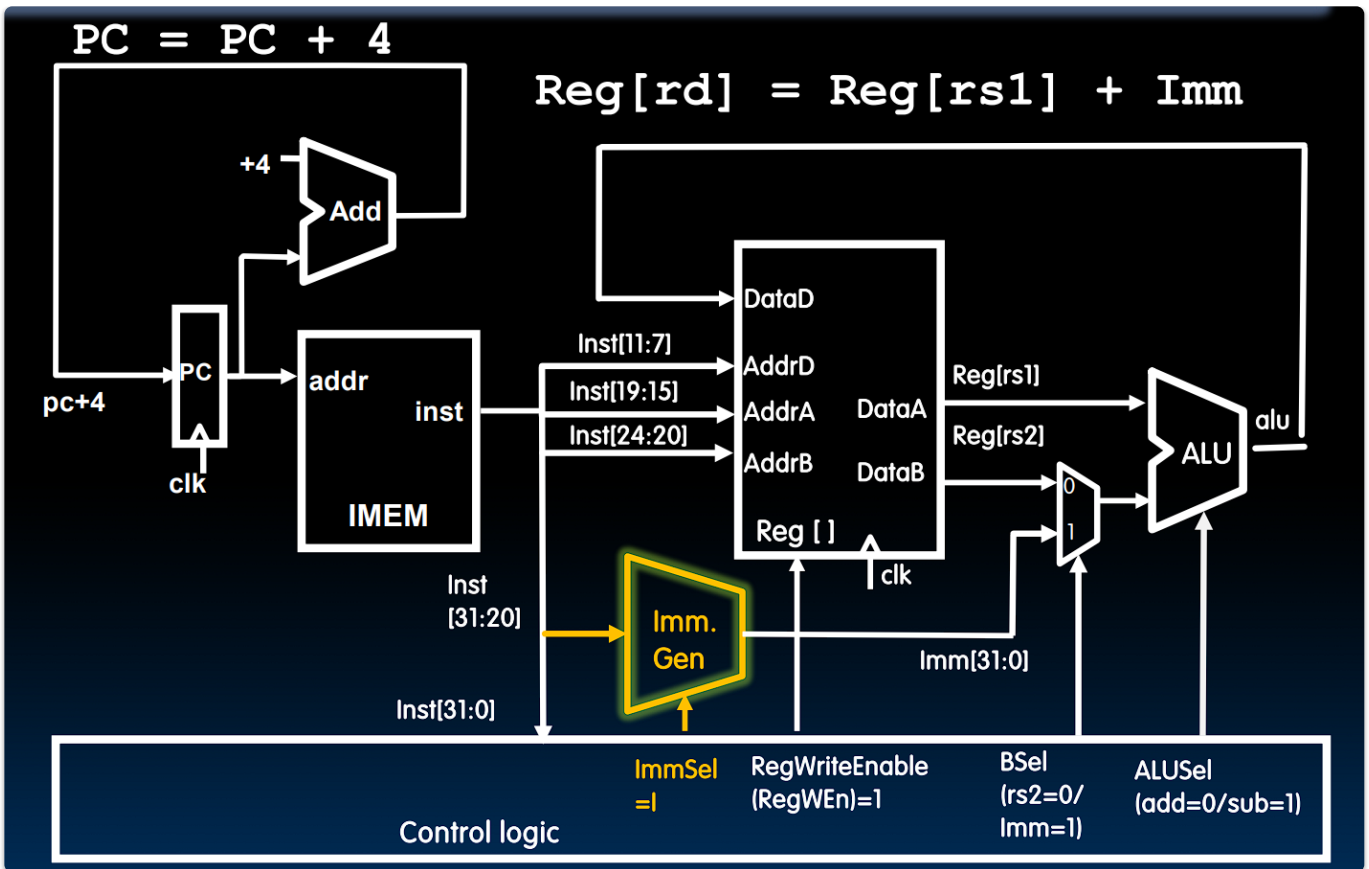

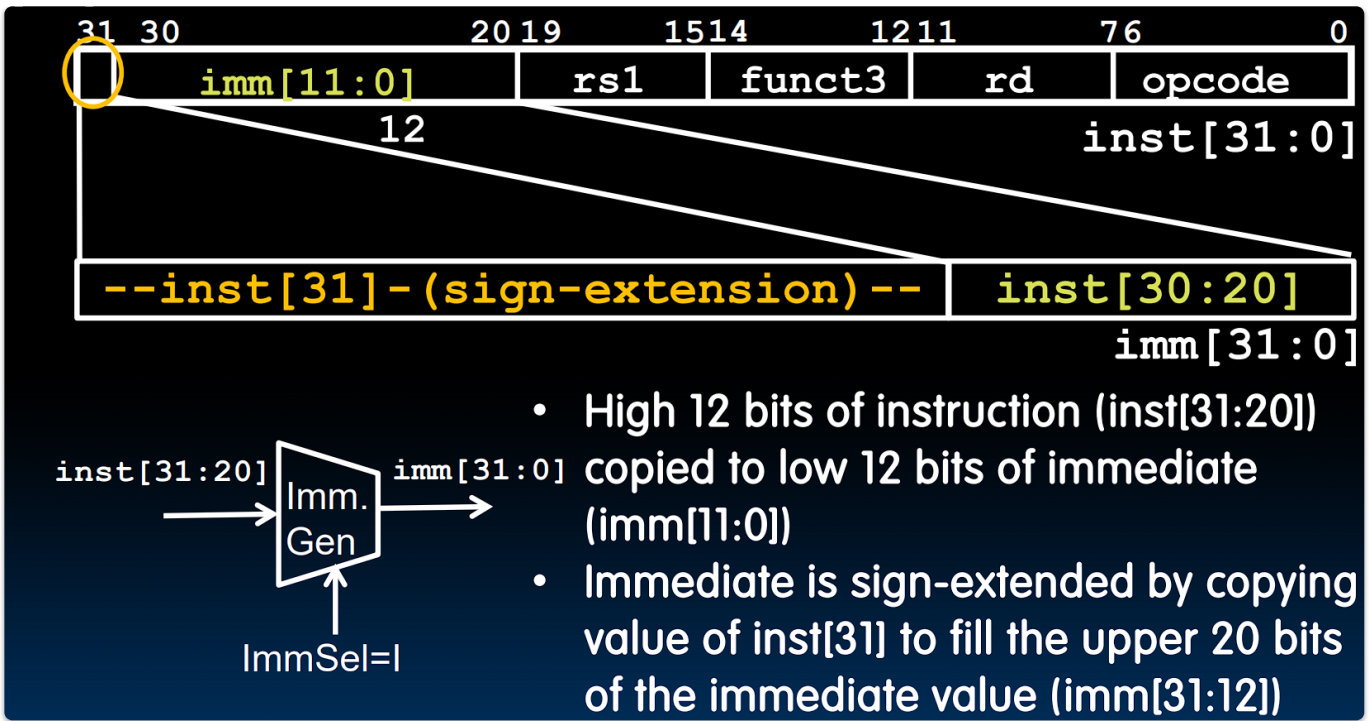


load

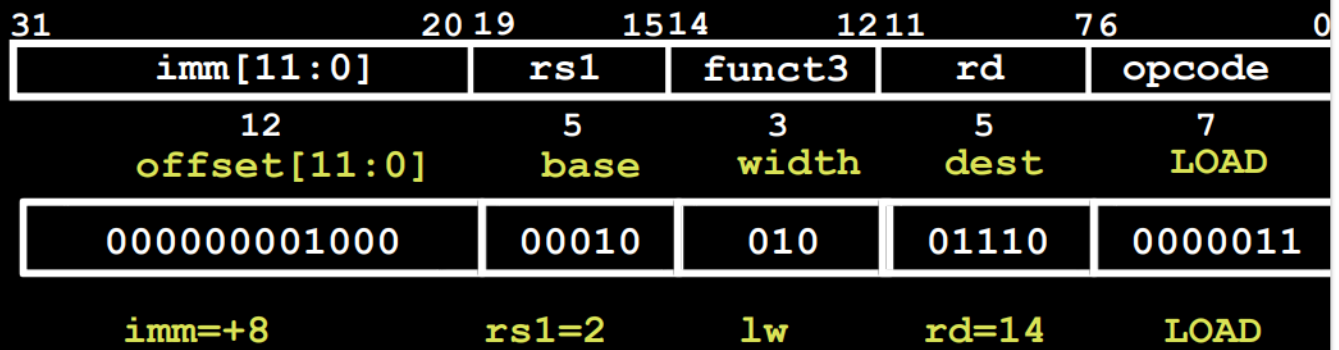
- RISC-V Assembly Instruction (I-type): `lw x14, 8(x2)`



- The 12-bit signed immediate is added to the base address in register `rs1` to form the **memory** address
  - This is very similar to the add-immediate operation but used to create address not to create final result

## R+I Arithmetic/Logic Datapath

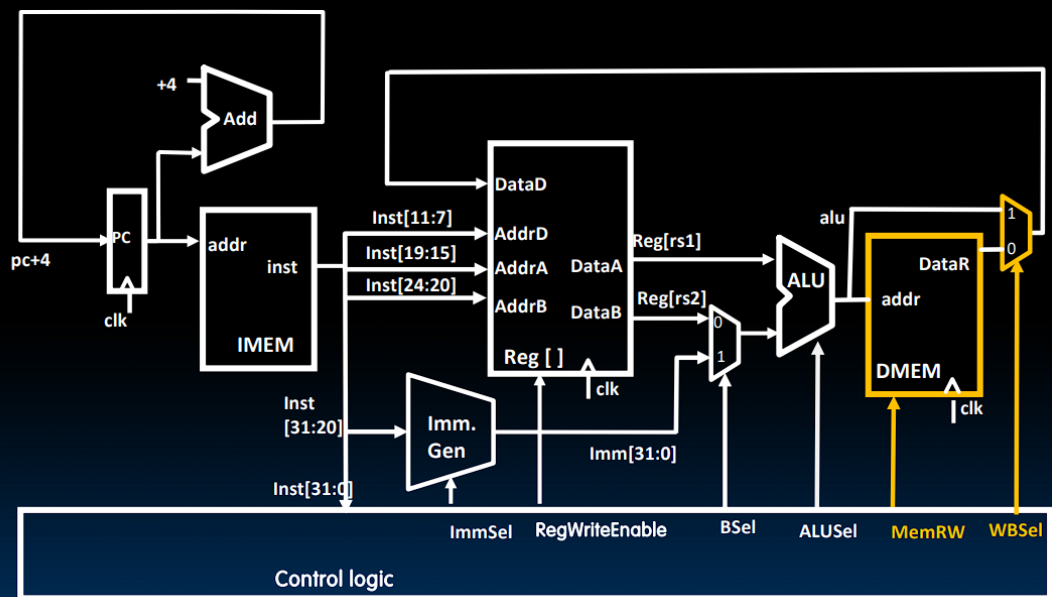

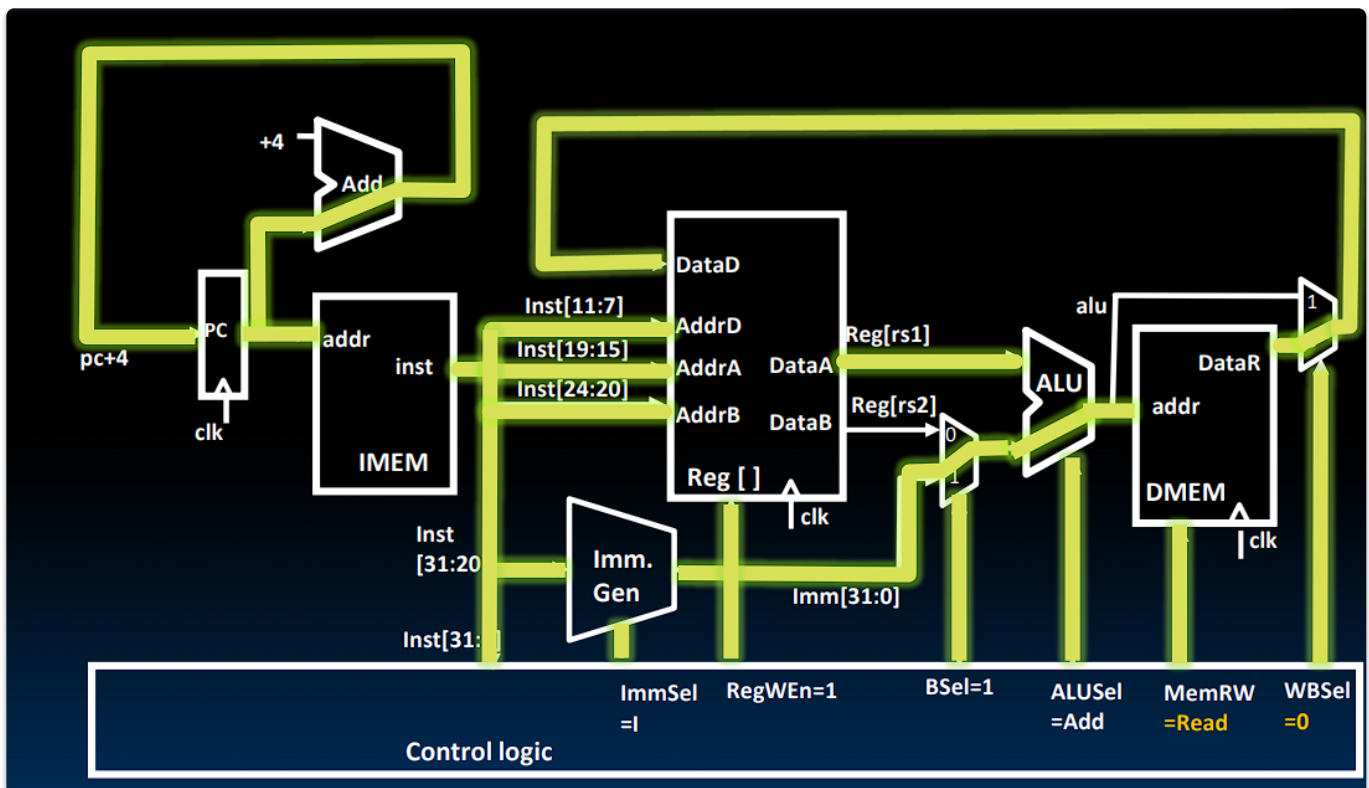

imm[11:0]	rs1	000	rd	0000011	lb
imm[11:0]	rs1	001	rd	0000011	lh
imm[11:0]	rs1	010	rd	0000011	lw
imm[11:0]	rs1	100	rd	0000011	lbu
imm[11:0]	rs1	101	rd	0000011	lhu

func3 field encodes size and 'signedness' of load data



- Supporting the narrower loads requires additional logic to extract the correct byte/halfword from the value loaded from memory, and sign- or zero-extend the result to 32 bits before writing back to register file.
  - It is just a mux + a few gates

## S-Format

### ADDING SW INSTRUCTION


- **sw**: Reads two registers, rs1 for base memory address, and rs2 for data to be stored, as well immediate offset!

**sw x14, 8(x2)**

 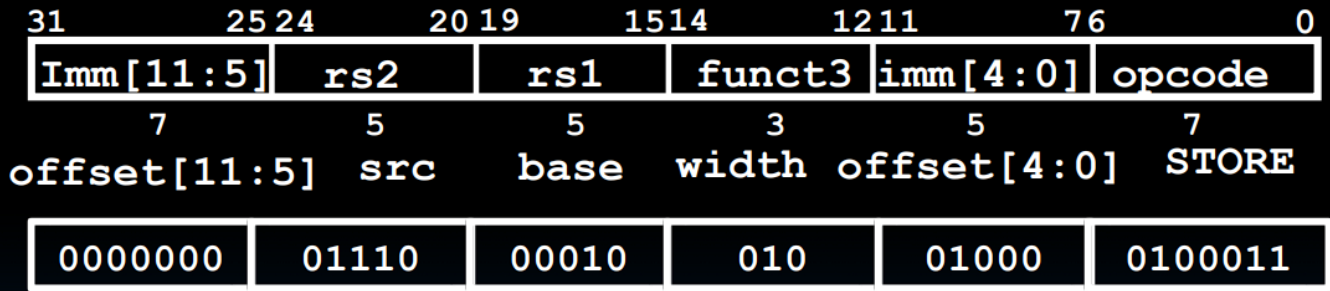


Garcia, Nikolic


## Adding sw to Datapath

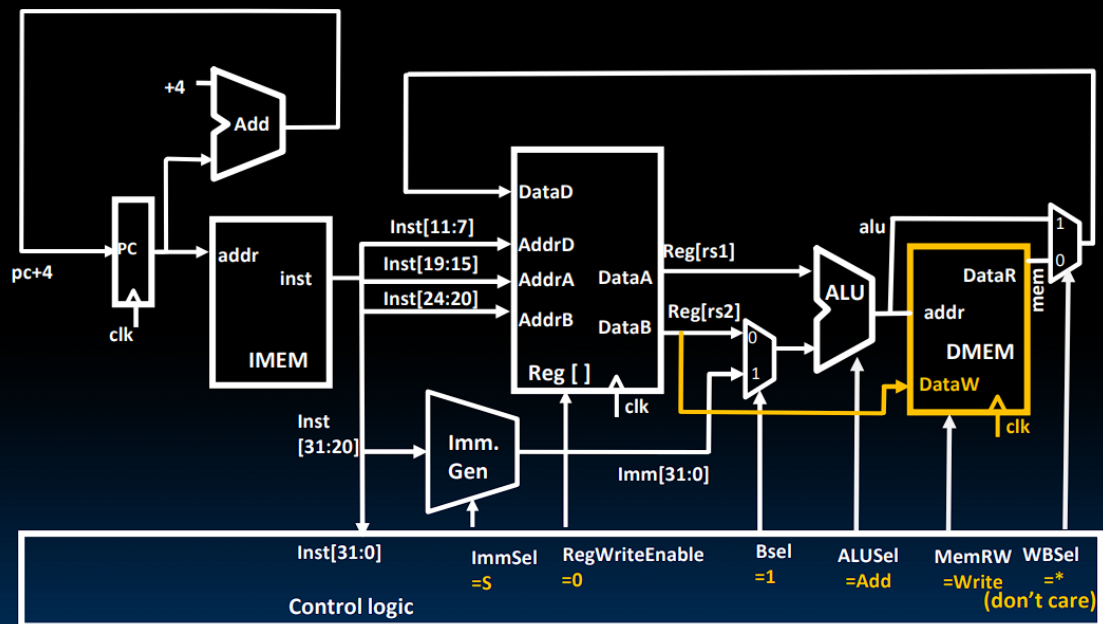

# Adding sw to Datapath

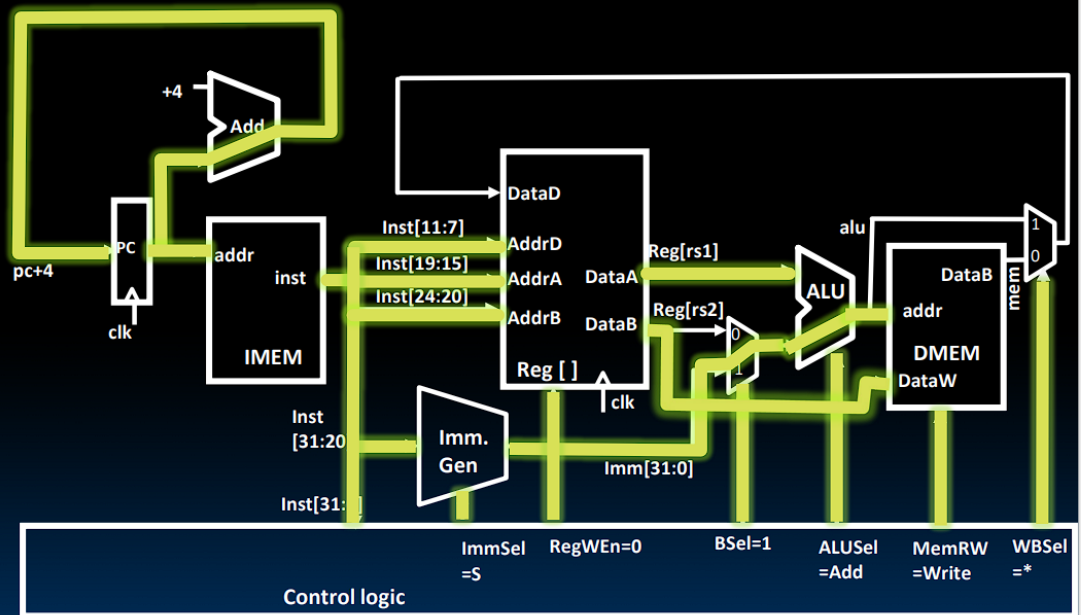


## I+S Immediate Generation

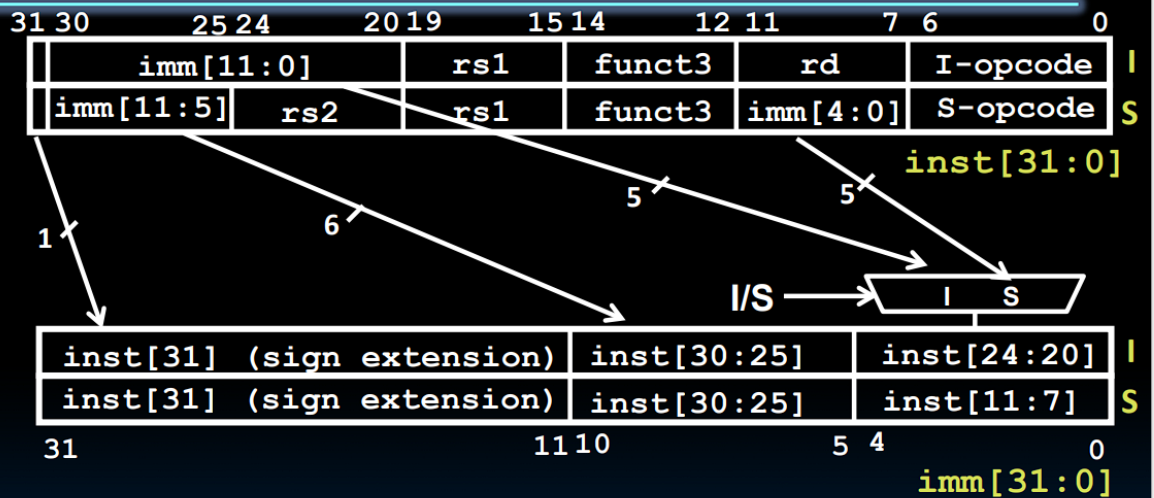


- Just need a 5-bit mux to select between two positions where low five bits of immediate can reside in instruction
- Other bits in immediate are wired to fixed positions in instruction

## B-Format

 


- B-format is mostly same as S-Format, with two register sources (**rs1/rs2**) and a 12-bit immediate **imm[12:1]**
- But now immediate represents values -4096 to +4094 in 2-byte increments
- The 12 immediate bits encode **even** 13-bit signed byte offsets (lowest bit of offset is always zero, so no need to store it)

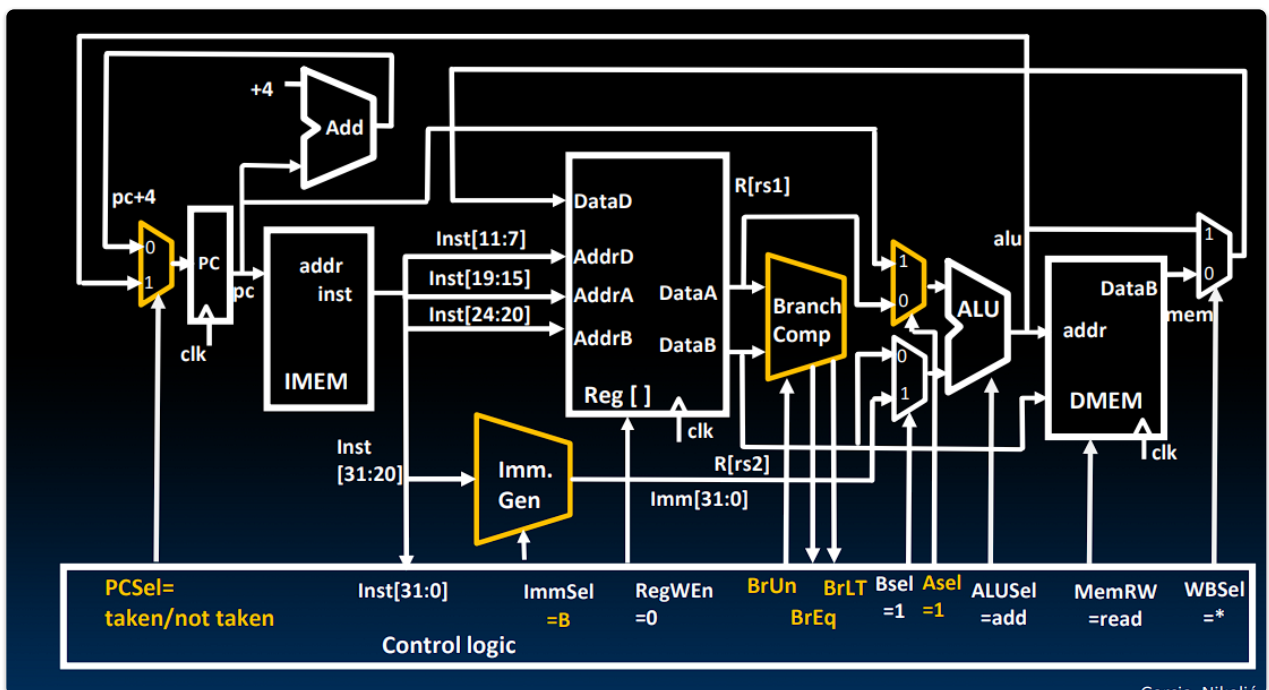- Need to compute **PC+IMMEDIATE** and to compare values of **rs1 and rs2**





# Branch Comparator

 

$\text{BrEq} = 1, \text{ if } A=B$

$\text{BrLT} = 1, \text{ if } A<B$

$\text{BrUn} = 1$  selects unsigned comparison for  $\text{BrLT}$ , 0=signed


$\overline{\text{BGE}}$  branch:  $A \geq B, \text{ if } \overline{A<B}$

$\overline{A<B} = \text{!(A<B)}$

Garcia, Nik

12-bit immediate encodes PC-relative offset of -4096 to +4094 bytes in multiples of 2 bytes

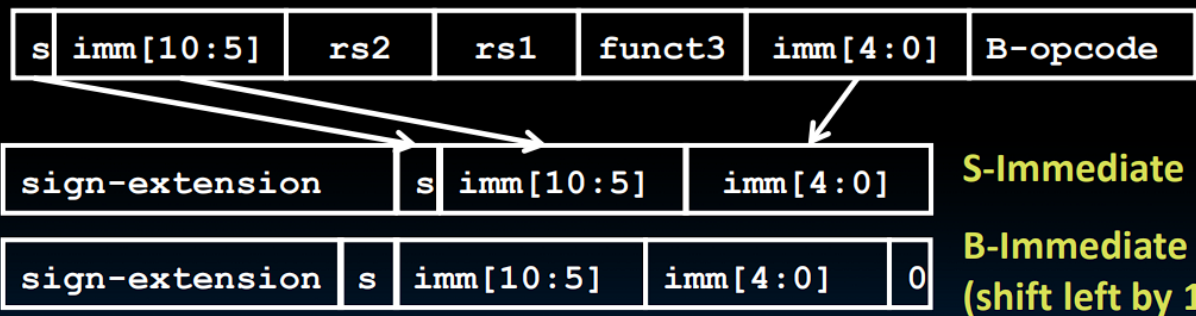Standard approach: Treat immediate as in range -2048..+2047, then shift left by 1 bit to multiply by 2 for branches



Each instruction immediate bit can appear in one of two places in output immediate value – so need one 2-way mux per bit

# Lighting Up Branch Path

